

Three Phase Full Wave Rectifier Using

Thyristors

Nabil Hesham Mohamed Rashad

52-11233

T-33

The German University in Cairo

Power Electronics ELCT704

I. Abstract


This report presents a comprehensive analysis and performance evaluation of three-phase full-wave rectifiers, a crucial component in power electronic systems for converting alternating current (AC) to direct current (DC). The study focuses on understanding the operational principles, characteristics of three-phase full-wave rectifiers, aiming to provide valuable insights about three phase full wave rectifiers. It covers operational principles; circuit topology and the impact of load variations are explored. The report includes experimental results and case studies to validate theoretical findings which were analyzed and simulated with MATLAB/SIMULINK.

II. Introduction

The necessity for effective power conversion in various industrial applications has led to a continual development in power electronic system technology. One of the key elements influencing this development is the three-phase full-wave rectifier, which is essential for converting alternating current (AC) to direct current (DC). In order to understand the intricacies of three-phase full-wave rectifiers' design, operating principles, and performance characteristics, this report explores them in great detail.

Rectification methods are particularly significant since industries are relying more and more on electronic devices that need steady DC power. One important component in satisfying these objectives is the three-phase full-wave rectifier, which has benefits in terms of efficiency, power quality, and flexibility to accommodate different load scenarios.

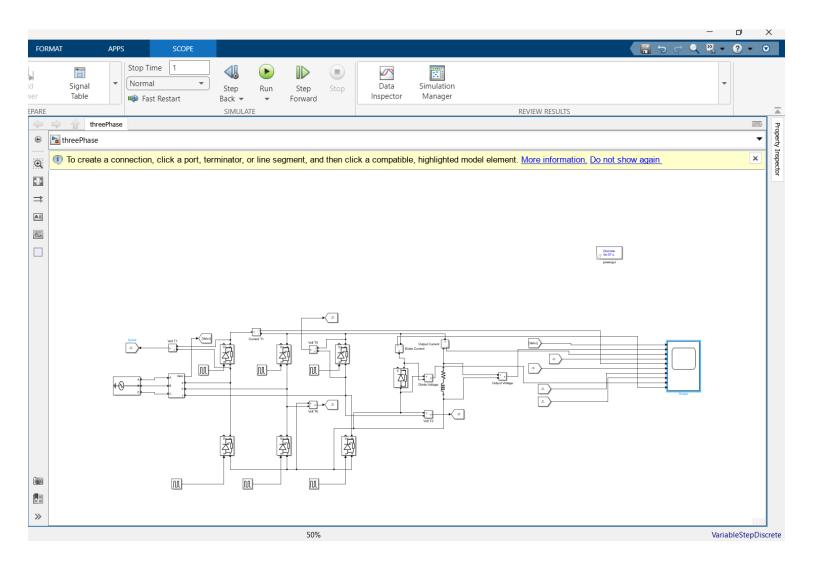
This report primarily focuses on the R load, RL load with varied firing angles, and RL with freewheeling diode. It contains just five case studies, all of which are significant. Other case situations are also there, but they are not taken into consideration.



III. Case Studies & Simulations

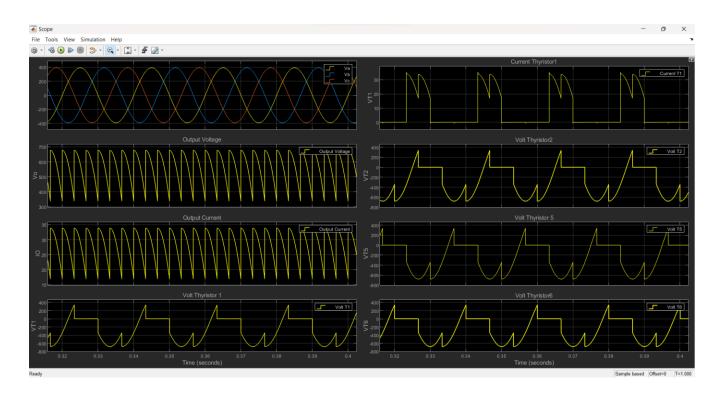
1. R Load (α =30) R = 10 Ω

A three-phase full-wave rectifier with a resistive load and a 30-degree firing angle is explored in this case study. The firing angle has an impact on the Thyristors' conduction timing, which in turn impacts the voltage and current waveforms and, in turn, performance indicators like efficiency, ripple factor, and average output voltage & RMS output voltage. The waveforms are shown in the figure below.



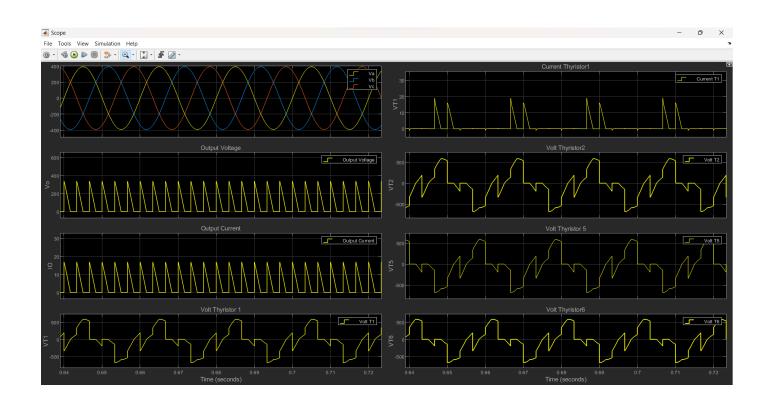2. R Load (α =90) R = 10 Ω


The performance of a three-phase full-wave rectifier with a resistive load and a 90-degree firing angle is examined in this case study. The firing angle significantly lowers average output voltage by affecting the Thyristors' performance measures like efficiency and ripple factor are to be assessed. The waveforms are shown in the figure below conduction timing.



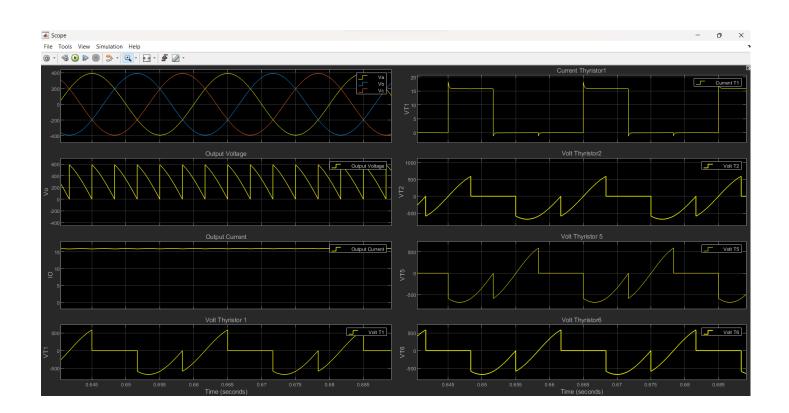3. RL Load (α =60) R = 10 Ω L =1H


This case study examines a three-phase full-wave rectifier at a firing angle of 60 degrees, with a resistive load and a highly inductive load. Analyzing voltage and current waveforms and assessing performance measures including average output voltage, ripple factor, and efficiency, the study looks at how the firing angle affects both kinds of loads. The waveforms are shown in the figure below.

Note: the current waveform may include some noises.



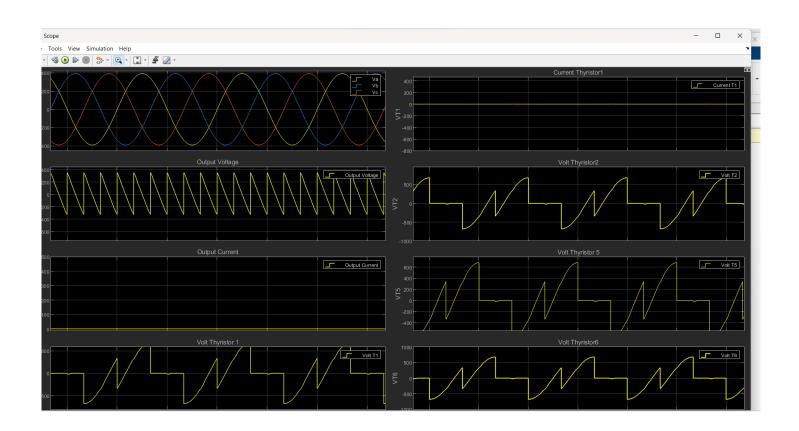4. RL Load (α =90) R = 10 Ω L =1H

This case study investigates a three-phase full-wave rectifier with resistive and highly inductive loads, focusing on a firing angle of 90 degrees. The analysis considers voltage and current waveforms, performance metrics like average output voltage and efficiency.



5. RL Load with Freewheeling diode (α =90) R = 10 Ω L =1H

The freewheeling diode provides an alternate path for the inductive current when the main diodes are not conducting. During the non-conductive phase of the main Thyristors, the inductive energy stored in the load seeks a path to discharge. The freewheeling diode allows this energy to circulate in a loop, preventing voltage spikes and protecting the circuit components. Note: the current waveform may include some noises.



IIII. Conclusion

The case studies conducted on three-phase full-wave rectifiers, spanning various load conditions and firing angles, provide valuable insights into the intricate dynamics of these critical components in power electronic systems. The diversity of scenarios explored, including resistive loads, highly inductive loads, and different firing angles, allows for a comprehensive understanding of their behavior in real-world applications.

The influence of firing angles on rectifier performance has been highlighted, showcasing how deliberate control over conduction timing affects crucial parameters such as average output voltage, ripple factor, and efficiency. The case studies with firing angles of 30, 60, and 90 degrees demonstrate the trade-offs involved in optimizing rectifier behavior based on specific application requirements.

The inclusion of resistive and highly inductive loads in the case studies expands the scope of analysis, reflecting the complexities faced in practical scenarios. The impact of inductance on power factor, and transient response has been thoroughly examined. Additionally, the introduction of freewheeling diodes in the context of inductive loads underscores the importance of protective measures to ensure stability and reliability in power electronics systems.

In conclusion, the collective findings from these case studies contribute significantly to the understanding of three-phase full-wave rectifiers. The knowledge gained is instrumental for optimizing designs, making informed decisions in system

configurations, and addressing challenges posed by various loads and operating conditions. As power electronic systems continue to evolve, the insights gleaned from these case studies opens the door to further improvements in efficiency, dependability, and versatility across a broad spectrum of applications as power electronic systems continue to develop.